

## PROTOTYPE VOLTAGE ALARM FOR BURN TESTER

This document contains information on how I constructed an alarm for use when burn testing scooter and light batteries.

The circuit is presented for information only, and should not be considered as a fully developed project. In particular I would change a number of things in a production/project version:

- use something like LM339 quad comparator for the Schmitt triggers rather than discrete components
- if retaining the 12V / 24V switch, put a separate over-voltage comparator circuit in to trigger the alarm if the unit is set to 12V operation with a 24V battery connected (this and the "OR" logic could probably all fit in the LM339)
- add some RF bypass capacitors at appropriate points
- replace the 24V pot with a 2:1 potential divider from the 12V output using a couple of higher precision or matched resistors, saving the cost of a 10 turn pot.

The objective was to make a circuit which is as simple and reliable as possible. One LED comes on when the circuit is connected to a battery, and a second LED and the rather loud piezo buzzer come on when that voltage drops below a set voltage, e.g. 10V or 20V. In use, the time is measured using a kitchen timer. I personally don't favour the idea of a fully automatic unit which disconnects the battery from the burn tester when the threshold is reached because:


- it would need a big relay - that could be one of the relays used in the scooters, except this would presumably not operate at 12V, or one could use an auto one
- if the relay sticks on, then the circuit won't work
- there would need to be an internal timer which stopped when the unit disconnected
- its still a good idea to monitor the battery voltage during the test, as the most common feature I have seen is a 2V drop in one of the battery voltages early in the test due to a dud cell in one battery, and the burn time alone doesn't tell you this is happening.

The circuit doesn't use batteries to operate, but does include a separate digital panel meter and battery (the PM128 datasheet says its power supply should be floating w.r.t. its inputs - probably this could be achieved with some suitable trickery/experimentation without using a separate battery, but for me it was easier just to put a battery in). The DPM isn't necessary and is just there for convenience - it saves forgetting to turn a separate DVM off etc.

The Schmitt trigger circuit is explained on [www.play-hookey.com/digital/experiments/rtl\\_schmitt.html](http://www.play-hookey.com/digital/experiments/rtl_schmitt.html)

I modified the values for just a couple of percent hysteresis.

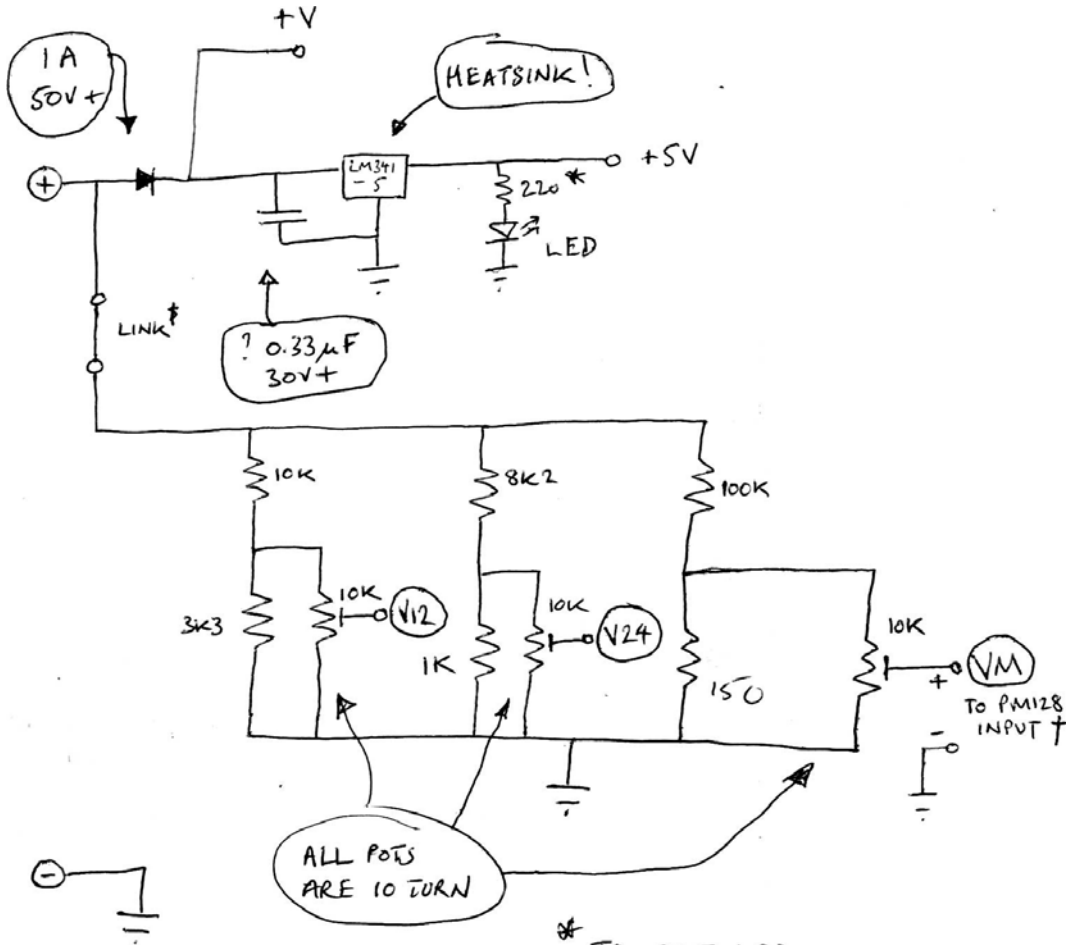**+5V Power Supply and voltage dividers for 12V, 24V and DPM**




\* TO SUIT LED

† Link "P1" on PM128 for decimal point  
 Power PM128 from 9V battery via pushbutton switch

‡ I put this in so I could apply separate voltage for setup - not necessary
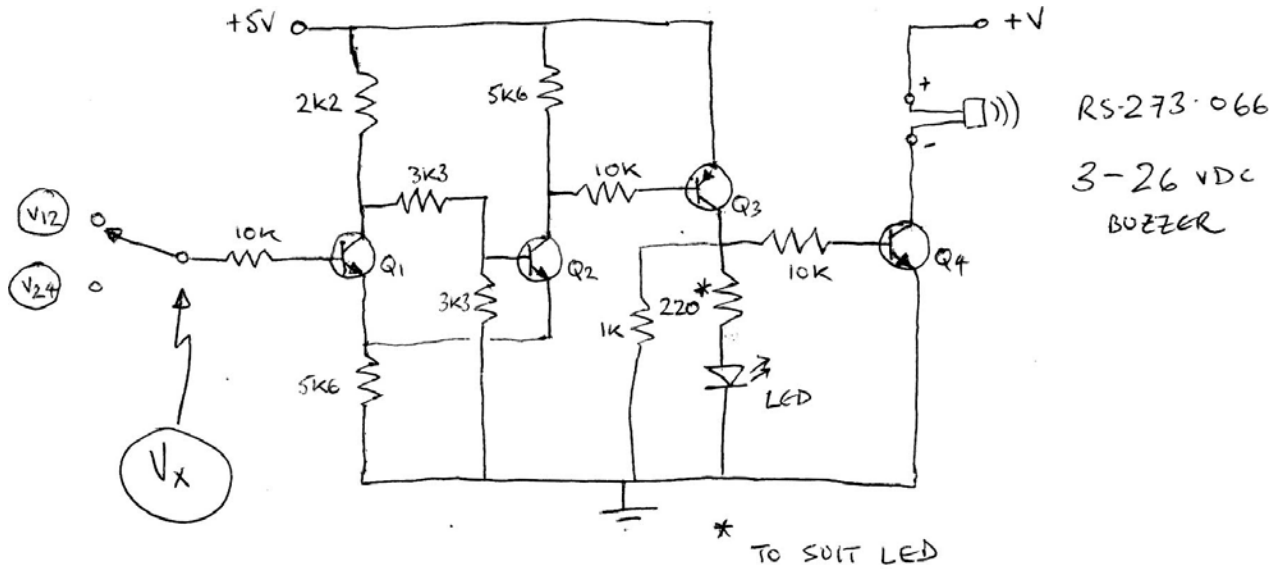
## Schmitt Trigger, Inverter and Buzzer Driver



N.B. SOME R.F. BYPASS CAPACITORS WOULD BE A VERY GOOD IDEA!!

Q<sub>1</sub> - Q<sub>4</sub> GENERAL PURPOSE SILICON  
(Q<sub>3</sub> = PNP)

### Setup Procedure


#### SETUP

1. Apply voltage  $V_s$  and measure  $V_x$  with DVM
2. Adjust relevant pot until alarm triggers @  $V_x = V_{XT}$  say
3. Adjust pot until:

$$V_x = \frac{V_{XT} \cdot V_s}{V_T}$$

where  $V_T$  = desired trigger voltage  
(e.g. 10V or 20V)

## Prototype with Kitchen Timer

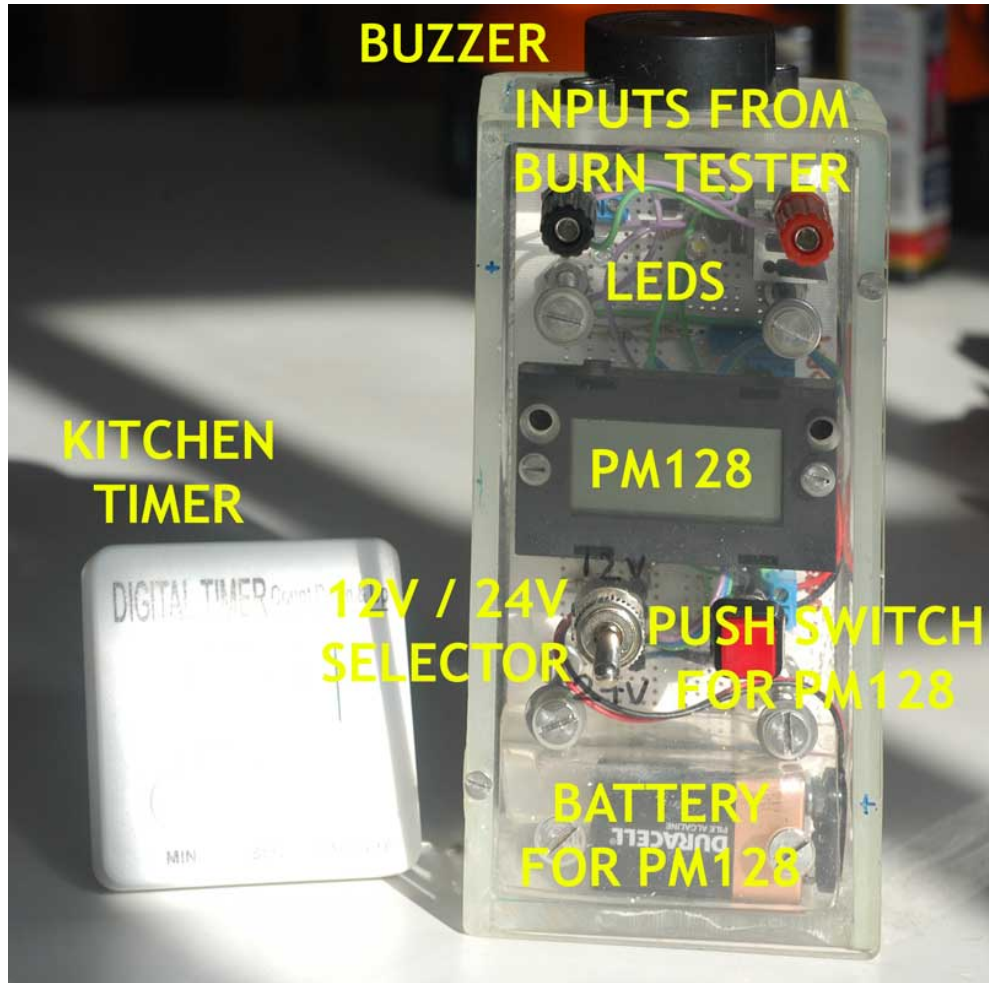

### Piezo Buzzer


(Note that this gets the full battery voltage across it, so must be 24V+ rated)



## Link on PM128 to Display Decimal Point




## Transistor Circuitry

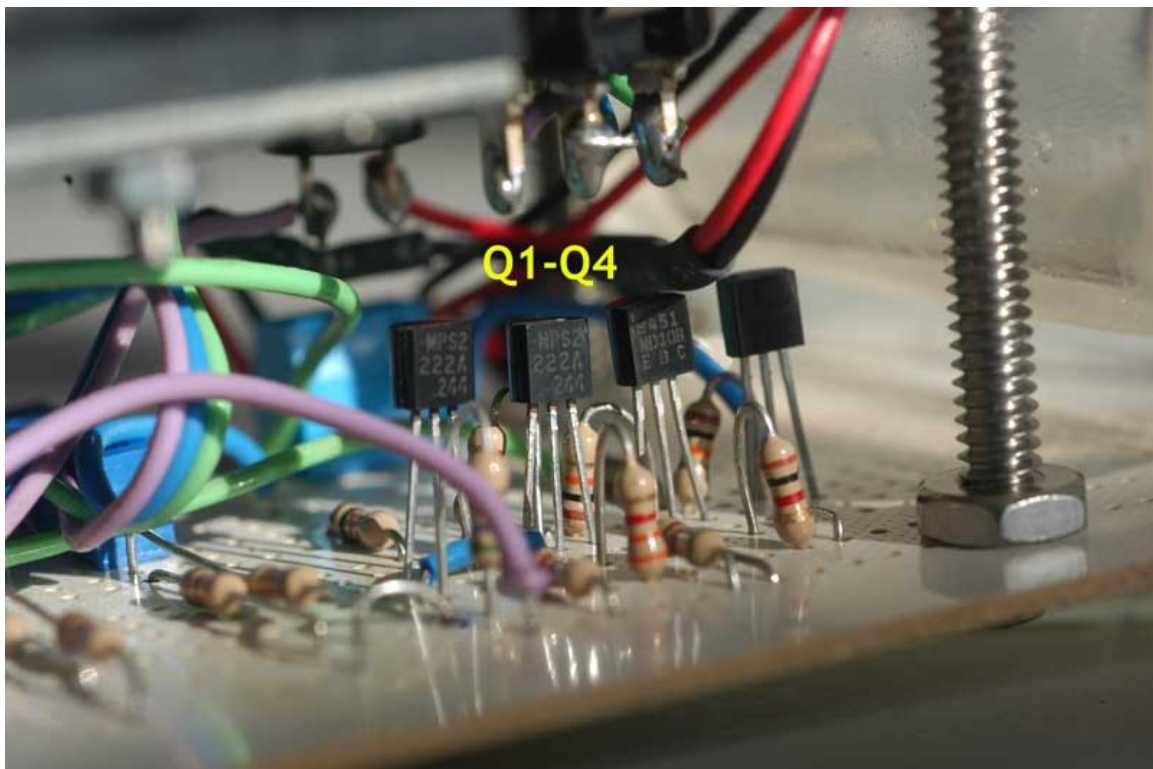



## Power Supply Arrangements and LEDs

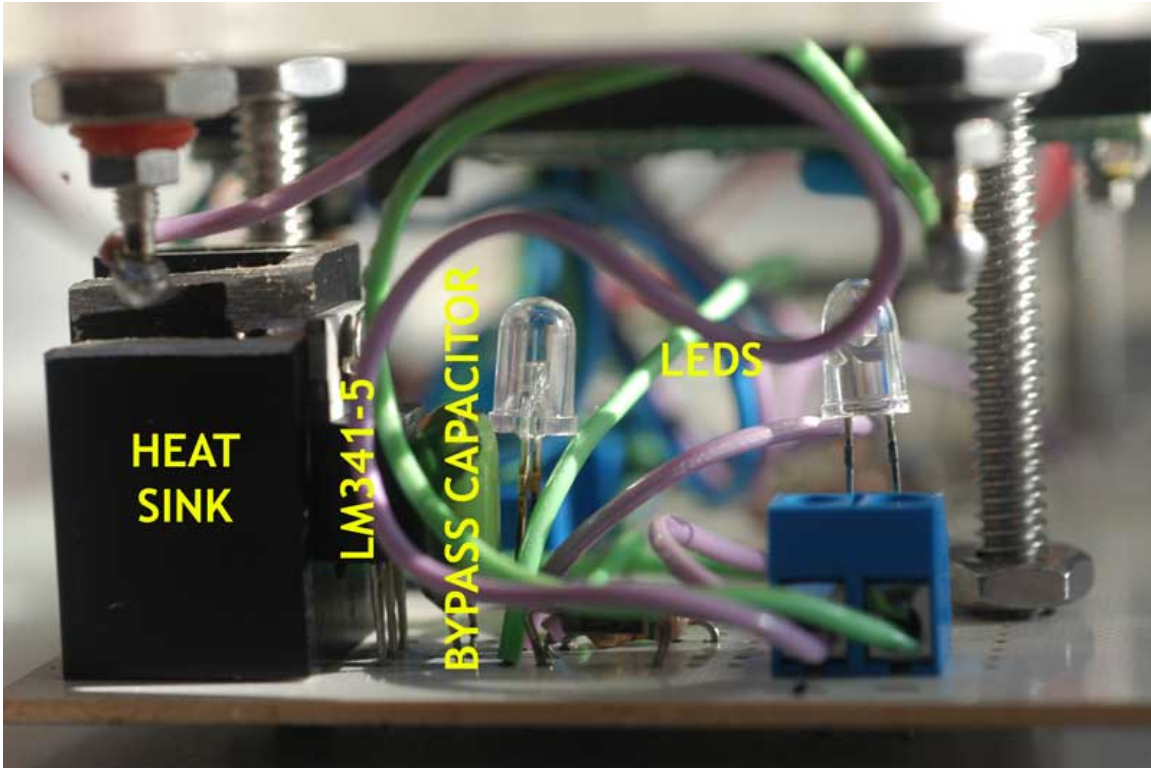

## Multi-turn Pots for Voltage Dividers

